


Analog to Digital Conversion

Frank Walsh

Definition & Necessity


Most signals we want to process are analog

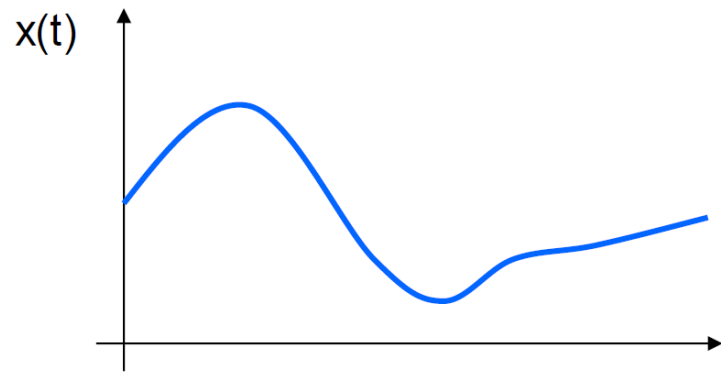i.e.: they are continuous and can take an infinity of values




Digital systems require discrete digital data

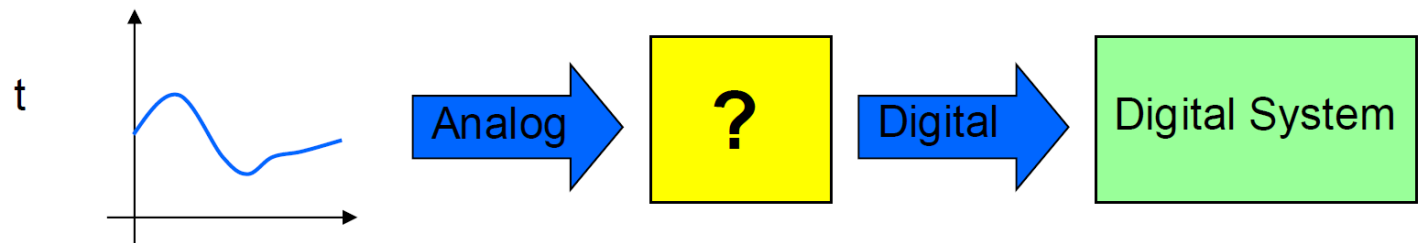ADC converts an analog information into a digital information




Applications

Voltmeter

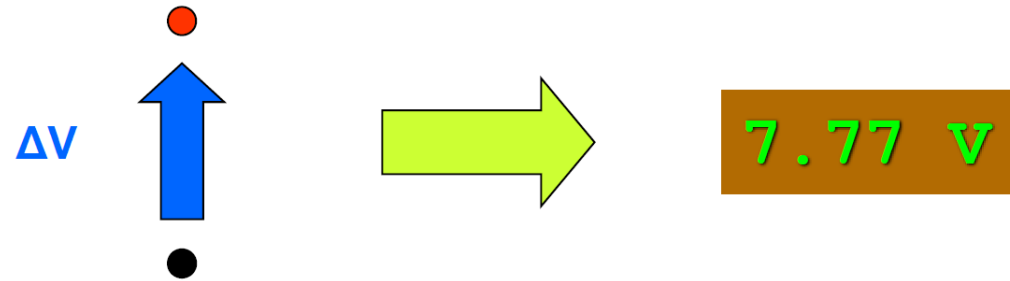

- Cell phone (microphone)

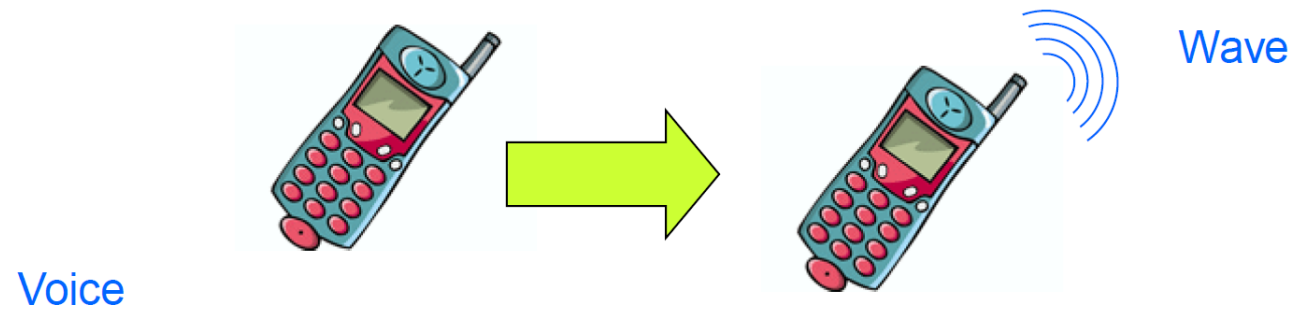

Analog to Digital Conversion Process

3 steps:

Sampling

Quantification

Coding


These operations are all performed in a same element:
the A to D Converter

Conversion Process: Sampling

Digital system works with discrete states

The signal is only defined at determined times

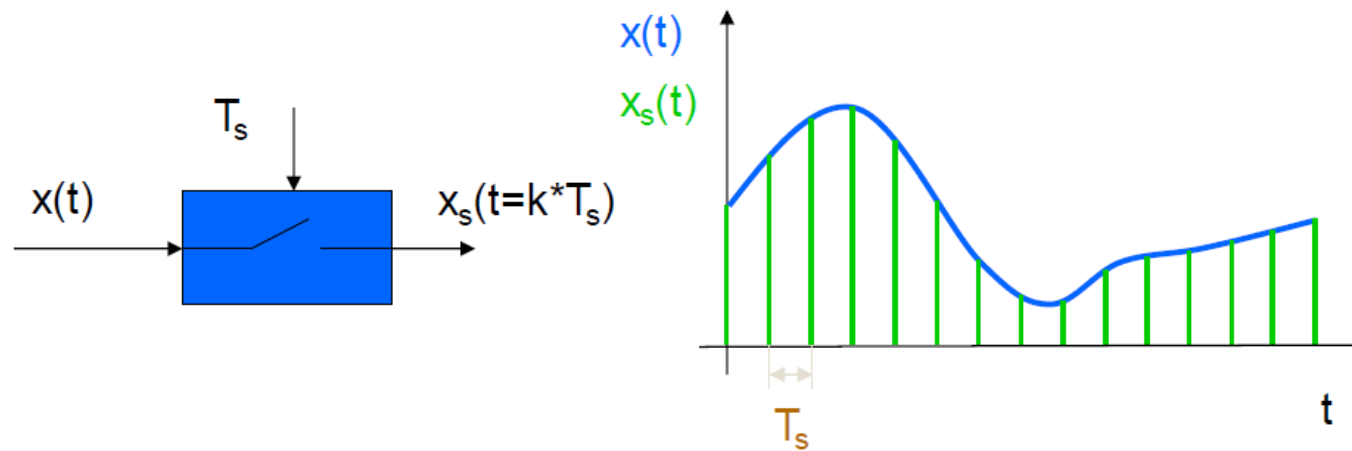The sampling times are proportional to the sampling period (T_s)



Conversion Process: Quantification

The signal can only take determined values


Belonging to a range of conversion (ΔV_r)

Based on number of bit combinations that the converter can output

Number of possible states:

$N=2^n$ where n is number of bits


Resolution: $Q = \Delta V_r / N$

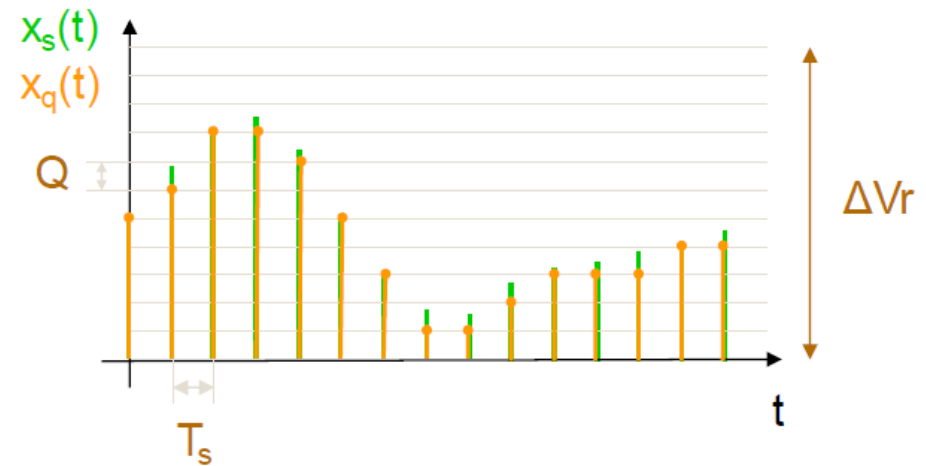

Conversion Process: Coding

Assigning a unique digital word to each sample

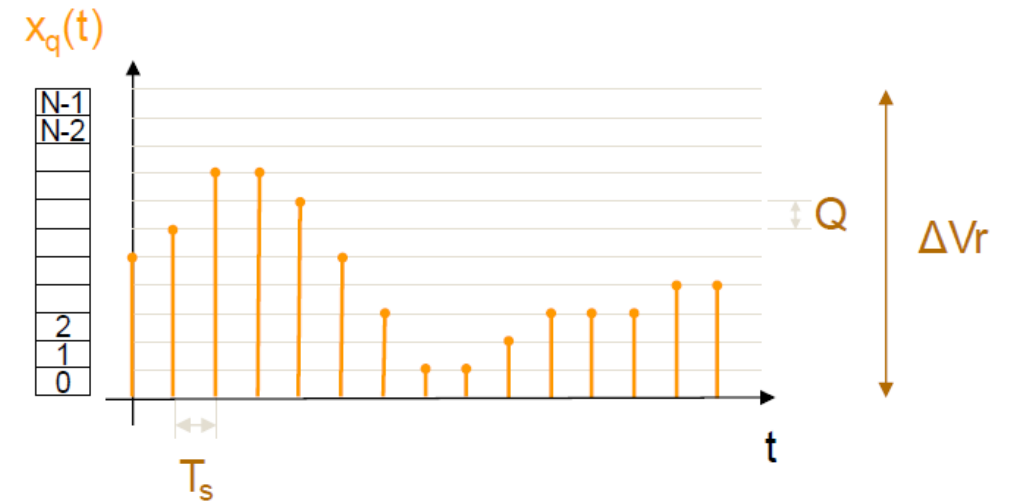Matching the digital word to the input signal



Types of ADC

- ❖ Flash ADC
- ❖ Sigma-delta ADC
- ❖ Successive approximation converter

Flash ADC

<https://www.analog.com/en/technical-articles/understanding-flash-adcs.html>

- Uses a linear voltage ladder with a comparator at each "rung" of the ladder to compare the input voltage to successive reference voltages.
- The output of these comparators is generally fed into a digital encoder, which converts the inputs into a binary value

Advantages

Very fast


Disadvantages

Needs many parts (255 comparators for 8-bit ADC)

Lower resolution


Expensive

Large power consumption

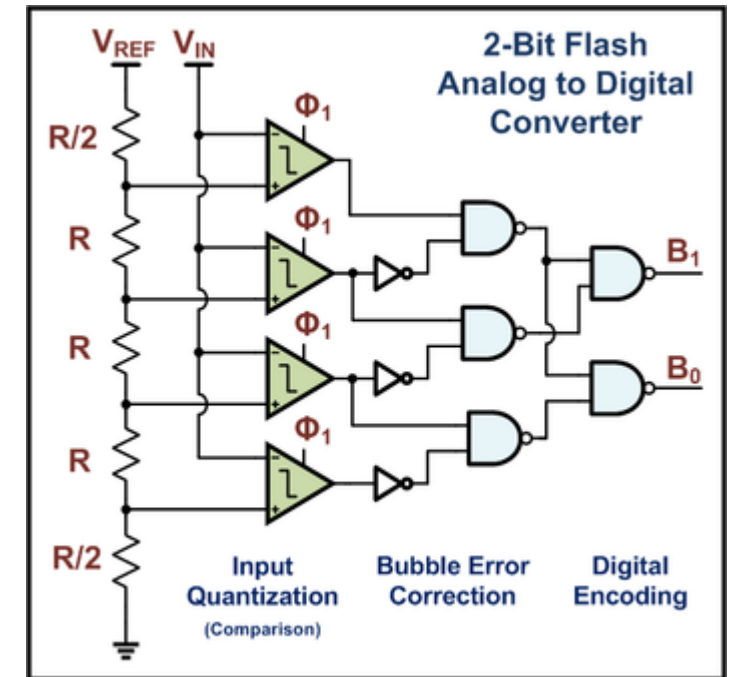

Sigma-Delta ADC

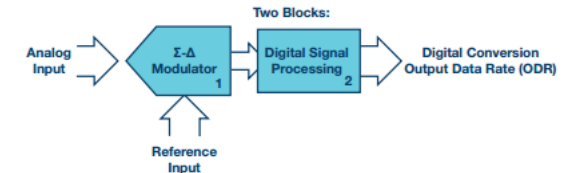- Typically there are two parts:
 - the Σ - modulator
 - digital signal processing block, usually a digital filter.
- More info here: <https://www.analog.com/en/design-center/interactive-design-tools/sigma-delta-adc-tutorial.html>



Advantages


High resolution
No precision
external
components
needed

Disadvantages


Slow due to
oversampling

Successive Approximation ADC

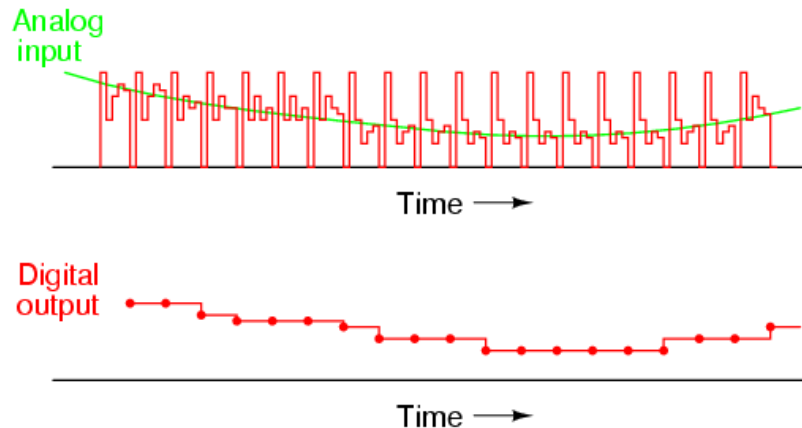
- Sets most significant bit (e.g. 0b1000)
- Converts to analog using DAC
- Compares guess to input
- Sets bit
- Moves to next bit
- Operates by successively dividing the voltage range by half.



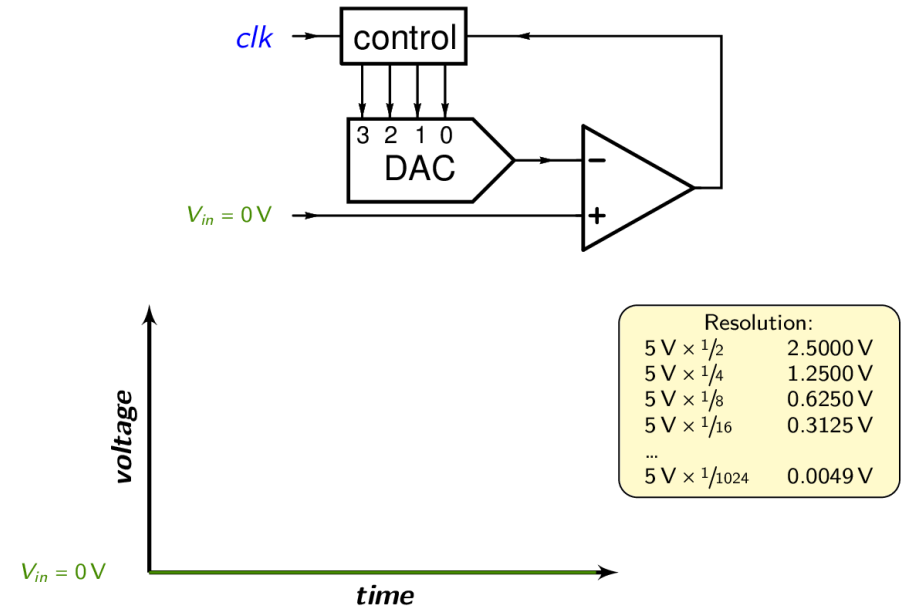Successive Approximation – example of a 4-bit ADC



Comparison of ADC Types

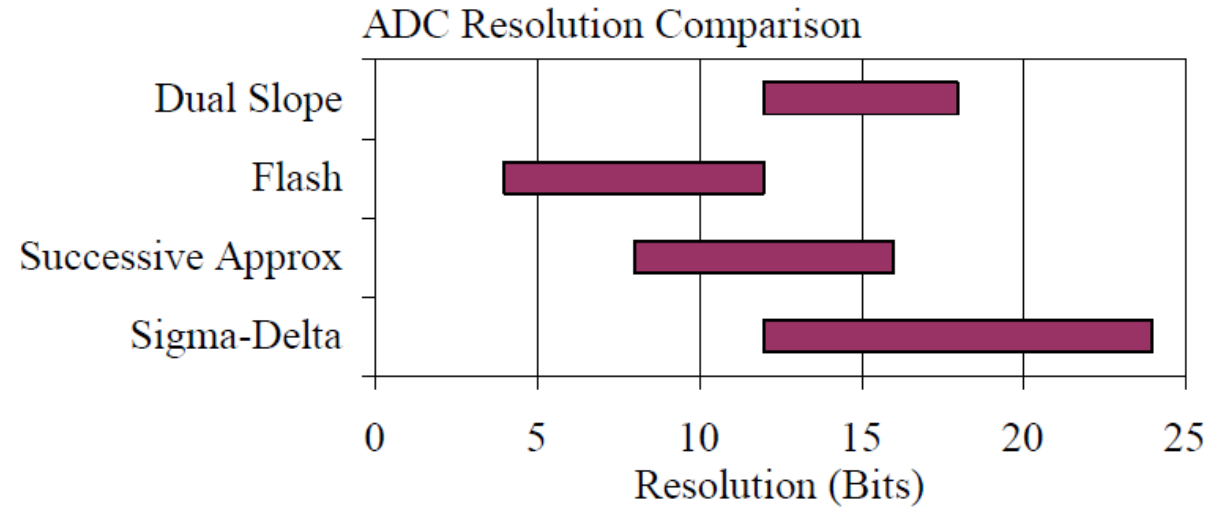

Type	Speed (relative)	Cost (relative)
Dual Slope	Slow	Med
Flash	Very Fast	High
Successive Approx	Medium – Fast	Low
Sigma-Delta	Slow	Low